

ASSIGNMENT-3

M Sai Santhosh Kumar

santhoshmandarapu1221@gmail.com

IITH - Future Wireless Communications (FWC)

CONTENTS

- 1 Question
- 2 Components
- 3 Truth Table
- 4 Logical Diagram
- 5 Implementation


3 TRUTH TABLE

1	a	b	c	z
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Truth table Boolean Function "z"

1 QUESTION

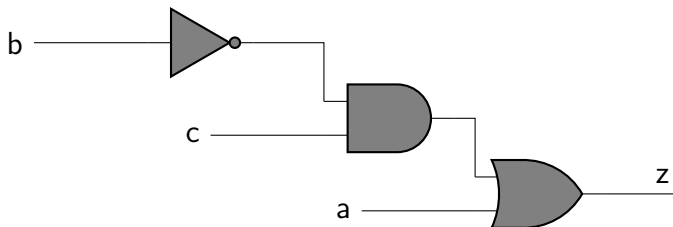Consider the Boolean function $z(a,b,c)$ Which of the



4 LOGICAL DIAGRAM

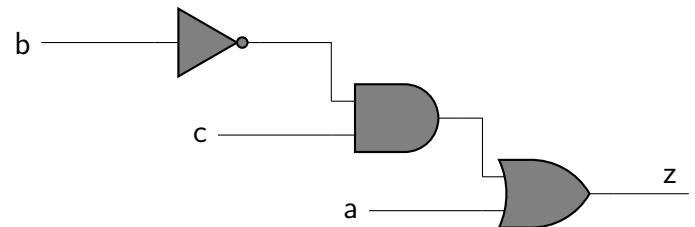


Fig. 1: Logical Diagram

following minterm lists represents the circuit given above?

- 1) $z = \sum(0, 1, 3, 7)$
- 2) $z = \sum(1, 4, 5, 6, 7)$
- 3) $z = \sum(2, 4, 5, 6, 7)$
- 4) $z = \sum(2, 3, 5)$

2 COMPONENTS

Component	Values	Quantity
Arduino	UNO	1
JumperWires	M-M	6
Breadboard		1
LED		1
Resistor	220ohms	1

Figure.a

5 IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	a	
3	b	
4	c	
5		z

Connections

a) Procedure

1. Connect the circuit as per the above table.
2. Connect the one end of the resistor to anode of LED and cathode of LED to ground.
3. Connect the output pin to another end of resistor.

4. Connect inputs to Vcc for logic 1, ground for logic 0.
5. Execute the circuit using the below code.

<https://github.com/santhosh-1221/cs282020/blob/main/code/code.asm>

6. Change the values of a,b,c in the code and verify the Truth Table.